

(6 pages)

Reg. No. :

Code No. : 1712

Sub. Code : R 4 CS 11/
B 4 CS 11

B.Sc. (CBCS) DEGREE EXAMINATION,
NOVEMBER 2010.

First Semester

Computer Science — Allied

Paper I — DIGITAL DESIGN

(For those who joined in July 2008 and afterwards)

Time : Three hours

Maximum : 75 marks

SECTION A — (10 × 1 = 10 marks)

Answer ALL questions.

Choose the correct answer.

1. DVD stands for —————

- (a) Digital Video Disk
- (b) Digital Versatile Disk
- (c) Data Versatile Disk
- (d) None

2. The 2's complement of 0110111 is —————

- (a) 1001000
- (b) 1001001
- (c) 10001001
- (d) 1000110

3. ANDing maxterms is denoted by —————

- (a) π
- (b) Σ
- (c) S
- (d) None

4. ECC stands for —————

- (a) Emitter coupled logic
- (b) Emitted-coupled logic
- (c) Emitted-couple logic
- (d) None

5. ————— is a universal gate

- (a) NAND
- (b) OR
- (c) AND
- (d) NOT

6. The circuit that checks the parity at the receiver is called a —————

- (a) parity checker
- (b) parity generator
- (c) parity corrector
- (d) none

7. The combinational circuit that converts n -input line to a maximum of 2^n unique output lines is _____

(a) decoder (b) encoder
(c) multiplexer (d) none

8. Storage elements that operate with signal level and controlled by a clock transition are called _____

(a) flip flops (b) latches
(c) clock control (d) none

9. A group of flip flop is called _____

(a) counter (b) register
(c) latch (d) none

10. The BCD counter counting from 0 to 9 is called _____

(a) deci counter (b) decade counter
(c) round counter (d) none

SECTION B — (5 × 5 = 25 marks)

Answer ALL the questions choosing either (a) or (b).

11. (a) Write about octal and hexadecimal numbers.

Or

- (b) Prove :

(i) $x + x = x$

(ii) $x \cdot x = x$

(iii) $x + 1 = 1$

12. (a) Explain sum of minterms with suitable example.

Or

- (b) Draw the logic diagrams for the Boolean expressions.

(i) $Y = A + B + B' + (A + C')$

(ii) $Y = (A \oplus C)' + B$

13. (a) Explain multilevel NAND circuit.

Or

- (b) Explain binary subtractor.

14. (a) Write about sequential circuits.

Or

- (b) Discuss about (i) state diagram (ii) state table.

15. (a) Explain registers with parallel load.

Or

- (b) Write notes on ring counter and up/down binary counter.

SECTION C — (5 × 8 = 40 marks)

Answer ALL the questions choosing either (a) or (b).

16. (a) Explain the steps involved in converting binary numbers to other bases.

Or

- (b) Discuss about Boolean functions in detail.

17. (a) Explain different forms of representing a boolean function.

Or

- (b) Convert each of the following to other canonical form :

(i) $F(x, y, z) = \Sigma(2, 5, 6)$

(ii) $F(A, B, C, D) = \pi (0, 1, 2, 4, 7, 9, 12)$

18. (a) Explain the analysis procedure of combinational circuit.

Or

- (b) Explain binary multiplier with a neat diagram.

19. (a) Explain in detail about decoders.

Or

- (b) Explain in detail - Analysis with JK flip flop.

20. (a) What is shift register? Explain about universal shift register.

Or

- (b) Explain in detail about ROM.