Reg. No. :

Code No. : 5551

Sub. Code : KPHM 13/ PPHM 13

M.Sc. (CBCS) DEGREE EXAMINATION, NOVEMBER 2020.

First Semester

Physics

INTEGRATED ELECTRONICS

(For those who joined in July 2016 and afterwards)

Time : Three hours

Maximum : 75 marks

PART A — $(10 \times 1 = 10 \text{ marks})$

Answer ALL questions.

Choose the correct answer :

- 1. In an enhancement MOSFET the conductivity of the channel
 - (a) Increases (b) Decreases
 - (c) Zero (d) None

(7 pages)

- 2. Triac is an ———— switch
 - (a) DC (b) AC
 - (c) Mechanical (d) None
- 3. The circuit responds only when the clock is transition between its two voltage states
 - (a) Level triggering (b) Edge triggering
 - (c) RC triggering (d) None
- 4. _____ flip flops are needed to store 4 bit binary number
 - (a) 2 (b) 4
 - (c) 3 (d) None
- 5. The expected output wave form of the following circuit is ______



- (a) Square wave (b) Sine wave
- (c) Triangular wave (d) Spikes
 - Page 2 Code No. : 5551

freat	fi uencies but sto	lter pps h	circui nigh fre	t which passes low equencies
(a)	Low pass	1.	(b)	High pass
(c)	Band pass		(d)	None
The	duty cycle	is	alway	rs number between
(a)	0.0 and 0.5		(b)	0.0 and 1.0
(c)	0.0 and 1.5		(d)	0.0 and 2.0
mod tran of ca	ulation system smitted throug rrier wave Amplitude	1 in gh tł	which ne disci	digital information is rete frequency change
(a)	Frequency			
(\mathbf{c})	Amplitude ar	nd fr	eauena	NV
(d)	None	iu ii	equein	, y
Shie it pr	lding is only e ovides a low —	effec	tive ag	ainst electric fields if — path to ground
(a)	Capacitative		(b)	Impedance
(c)	Inductance		(d)	None
The quar	electrical tra ntity into an —	insd	ucer c	onverts the physical — signal
(a)	Electric		(b)	Magnetic
(c)	Ontical		(d)	Electromagnetic

Page 3 Code No. : 5551

PART B — $(5 \times 5 = 25 \text{ marks})$

Answer ALL questions choosing either (a) or (b).

Each answer should not exceed 250 words.

11. (a) Draw the circuit of an NAND DTL gates and explain its operation.

Or

- (b) Explain the operation of JK master/slave flip-flop with neat circuit diagram and truth table.
- 12. (a) Explain the operation of depletion MOSFET with diagram.

Or

- (b) Explain the construction and working of TRIAC.
- 13. (a) Sketch the sample and hold circuit and explain its operation.

 \mathbf{Or}

(b) Draw the circuit of an OP-amp integrator and explain its operation. Sketch the input and output waveforms.

> Page 4 Code No. : 5551 [P.T.O.]

14. (a) Draw the block diagram of IC 566 voltage controlled oscillator and explain its operation.

Or

- (b) Discuss the application of PLL IC for frequency multiplication.
- 15. (a) Write short note on Box-car integrator.

Or

(b) Write working principle of lock in amplifiers.

PART C — $(5 \times 8 = 40 \text{ marks})$

Answer ALL questions choosing either (a) or (b).

Each answer should not exceed 600 words.

- 16. (a) (i) Define sheet resistance R_s . What is the order of magnitude R_s for the base region and also for the emitter region? Sketch the cross-section of IC resistor
 - (ii) Describe a thin film resistor.

Or

(b) Explain theory and working of junction field effect transistor.

Page 5 **Code No. : 5551**

17. (a) Explain the action of JK flip-flop with neat circuit diagram and truth table. Also explain how the racing problem is avoided.

Or

- (b) (i) Write the advantages of a synchronous counter over a ripple counter.
 - (ii) Explain the construction and operation of a 4 bit ripple counter.
- 18. (a) Draw the circuit diagram of the instrumentation amplifier and explain its operation.

Or

(b) Solve the differential equation by analog computation.

$$\frac{d^2 V}{dt^2} + k_1 \frac{dv}{dt} + k_2 v - v_1 = 0.$$

19. (a) Explain how IC 555 can be used as an astable multivibrator with circuit diagram. Also explain why astable multivibrator is called as free running multivibrator.

Or

(b) Explain the process of FSK demodulation using PLL.

Page 6 **Code No. : 5551**

20. (a) Explain the AC signal conditioning system with the help of the block diagram.

 \mathbf{Or}

(b) Define noise with reference to electrical system. Classify and explain the noise sources.

Page 7 Code No. : 5551