

Reg. No. :

**Code No. : 20270 E Sub. Code : JACA 11/
SACA 11/AACA 11/
CACA11**

**B.C.A. (CBCS) DEGREE EXAMINATION,
NOVEMBER 2021**

First Semester

Computer Applications — Allied

DIGITAL DESIGN

(For those who joined in July 2016 onwards)

Time : Three hours Maximum : 75 marks

PART A — (10 × 1 = 10 marks)

Answer ALL questions.

Choose the correct answers :

1. The binary equivalent of decimal number 15 is
(a) 1101 (b) 1011
(c) 1111 (d) 1001
2. How many bits are byte
(a) 4 (b) 8
(c) 16 (d) 32

3. For n binary variables we can obtain _____ minterms.
(a) n (b) 2^n
(c) $2*n$ (d) n^2
4. A product of sums is a Boolean expression contains _____ terms.
(a) OR (b) AND
(c) not (d) sum
5. Combinational circuit has _____ an m outputs.
(a) n (b) m
(c) 2^n (d) $2*n$
6. A combinational circuit that performs the addition of two bits is called _____ adder.
(a) two (b) half
(c) full (d) binary
7. A _____ is a digital circuit that performs the inverse operation.
(a) encoder (b) decoder
(c) multiplexer (d) demultiplexer
8. An encode has n input lines 2^n input lines and _____ output lines.
(a) n (b) m
(c) 2^n (d) $2*n$
9. How many types of memory is available?
(a) 2 (b) 3
(c) 4 (d) 5

10. Which of the following is volatile memory?
- (a) RAM
 - (b) ROM
 - (c) Secondary storage
 - (d) None of these

PART B — ($5 \times 5 = 25$ marks)

Answer ALL questions, choosing either (a) or (b).

Each answer should not exceed 250 words.

11. (a) Describe about 1's complement and 2's complement numbers.

Or

- (b) Explain any five Boolean functions.

12. (a) Explain five variable map.

Or

- (b) Describe any three logic gates.

13. (a) Describe combinational circuits.

Or

- (b) Describe binary adder.

14. (a) Write short notes on Flip-flop.

Or

- (b) Describe sequential circuits.

15. (a) Write a note on binary counter.

Or

- (b) Explain memory unit with neat diagram.

PART C — ($5 \times 8 = 40$ marks)

Answer ALL questions, choosing either (a) or (b).

Each answer should not exceed 600 words.

16. (a) Explain various logic gates.

Or

- (b) Explain the conversion of octal number to decimal and hexa decimal.

17. (a) Explain four variable map.

Or

- (b) Simplify the following Boolean function using sum-of product method $F(A,B,C,D) = (0, 1, 2, 5, 8, 9, 10)$.

18. (a) Explain subtractor.

Or

- (b) Describe binary multiplier.

19. (a) Explain decoder.

Or

- (b) Describe storage element latches.

20. (a) Describe memory decoding.

Or

- (b) Explain error detection and correction.